
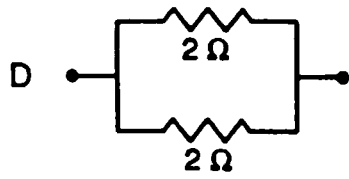


- 1 A copper wire is connected across a constant voltage source. The current flowing in the wire can be increased by increasing the wire's
- | | |
|------------------------|---------------|
| 1 cross-sectional area | 3 resistance |
| 2 length | 4 temperature |

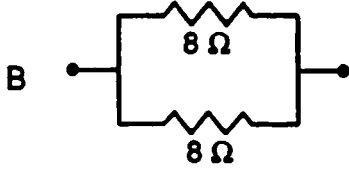- 2 Which two of the resistor arrangements shown below have equivalent resistance?




- | | |
|-------------|-------------|
| (1) A and B | (3) C and D |
| (2) B and C | (4) D and A |

- 3 A clothes dryer connected to a 240-volt line draws 30. amperes of current for 20. minutes (1,200 seconds). Approximately how much electrical energy is consumed by the dryer?
- | | |
|-------------------------|-------------------------|
| (1) 4.8×10^3 J | (3) 1.4×10^5 J |
| (2) 7.2×10^3 J | (4) 8.6×10^6 J |

- 4 A metal conductor is used in an electric circuit. The electrical resistance provided by the conductor could be increased by
- 1 decreasing the length of the conductor
 - 2 decreasing the applied voltage in the circuit
 - 3 increasing the temperature of the conductor
 - 4 increasing the cross-sectional area of the conductor

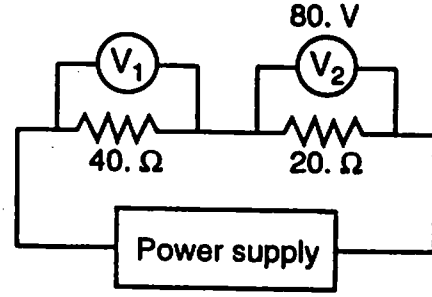
- 5 In the circuit shown below, voltmeter V_2 reads 80. volts.



What is the reading of voltmeter V_1 ?

- | | |
|-----------|-----------|
| (1) 160 V | (3) 40. V |
| (2) 80. V | (4) 20. V |

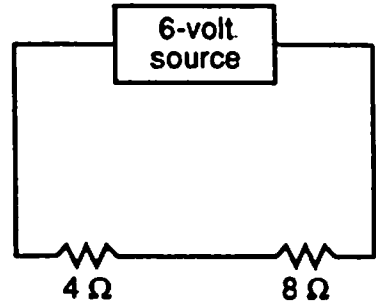- 6 The diagram below shows a circuit with two resistors.




Compared to the potential drop across the 8-ohm resistor, the potential drop across the 4-ohm resistor is

- | | |
|------------------|-----------------------|
| 1 the same | 3 one-half as great |
| 2 twice as great | 4 four times as great |

- 7 In a lightning strike, a charge of 18 coulombs is transferred between a cloud and the ground in 2.0×10^{-2} second at a potential difference of 1.5×10^6 volts. What is the average current produced by this strike?

- | | |
|----------------------------|-------------------------|
| (1) 3.6×10^{-1} A | (3) 3.0×10^4 A |
| (2) 9.0×10^2 A | (4) 7.5×10^7 A |

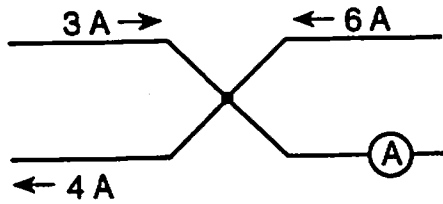
8 The diagram below shows the current in a segment of a direct current circuit.



What is the reading of ammeter A?

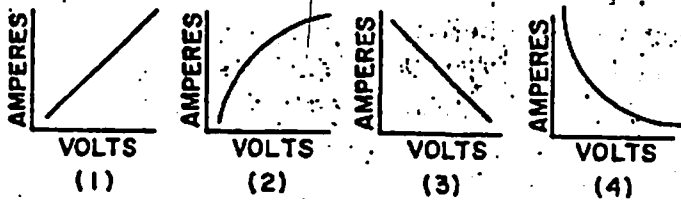- (1) 1 A
- (2) 5 A
- (3) 7 A
- (4) 8 A


9 Which graph best represents a material behaving according to Ohm's law?



10 Three resistances of 2 ohms, 4 ohms, and 6 ohms are connected in parallel. The equivalent resistance of the three resistors is

- 1 less than 2 ohms
- 2 between 2 ohms and 4 ohms
- 3 between 4 ohms and 6 ohms
- 4 greater than 6 ohms

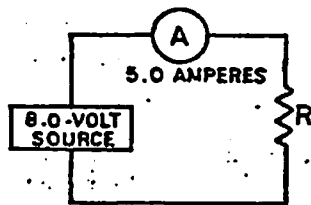11 The circuit represented in the diagram at the right is a series circuit. The electrical energy expended in resistor R in 2.0 seconds is



- (1) 20. J
- (2) 40. J
- (3) 80. J
- (4) 120 J


12 As the temperature of a metallic conductor increases, its resistance

- 1 decreases
- 2 increases
- 3 remains the same

13 An operating lamp draws a current of 0.50 ampere. The amount of charge passing through the lamp in 10. seconds is

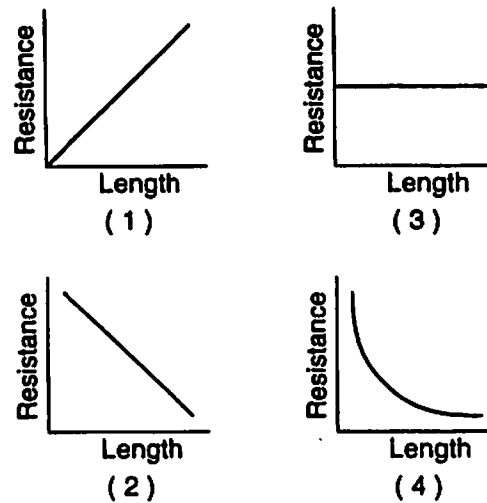- (1) 0.050 C
- (2) 2.0 C
- (3) 5.0 C
- (4) 20. C

14 Which graph best represents the relationship between the resistance of a copper wire of uniform cross-sectional area and the wire's length at constant temperature?



15 Which is a vector quantity?

- 1 electric charge
- 2 electrical resistance
- 3 electrical potential difference
- 4 electric field intensity


16 To increase the brightness of a desk lamp, a student replaces a 60-watt light bulb with a 100-watt bulb. Compared to the 60-watt bulb, the 100-watt bulb has

- 1 less resistance and draws more current
- 2 less resistance and draws less current
- 3 more resistance and draws more current
- 4 more resistance and draws less current

17 An electric dryer consumes 6.0×10^6 joules of energy when operating at 220 volts for 30. minutes (1800 seconds). During operation, the dryer draws a current of approximately

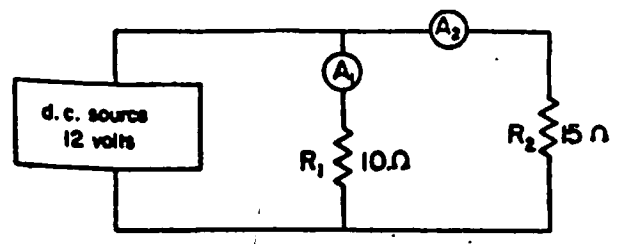- (1) 10. A
- (2) 15 A
- (3) 20. A
- (4) 25 A

Base your answers to questions 18 through 22 on the diagram below which represents an electrical circuit.




- 18 The equivalent resistance of the circuit is
 - (1) 25 Ω
 - (2) 6.0 Ω
 - (3) 5.0 Ω
 - (4) 0.17 Ω
- 19 The potential difference across R_2 is
 - (1) 1.0 V
 - (2) 2.0 V
 - (3) 10. V
 - (4) 12 V
- 20 The magnitude of the current in ammeter A_1 is
 - (1) 120 A
 - (2) 2.0 A
 - (3) 1.2 A
 - (4) 0.83 A

Note that questions 21 and 22 have only three choices.

- 21 Compared to the current in A_1 , the current in A_2 is
 - 1 less
 - 2 greater
 - 3 the same
- 22 If another resistance were added to the circuit in parallel, the equivalent resistance of the circuit would
 - 1 decrease
 - 2 increase
 - 3 remain the same

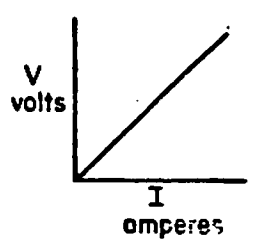- 23 The graph at the right shows how the voltage and current are related in a simple electric circuit. For any point on the line, what does the ratio of V to I represent?
 - 1 work in joules
 - 2 power in watts
 - 3 resistance in ohms
 - 4 charge in coulombs



Base your answers to questions 24 through 28 on the information below.


An electric heater rated at 4,800 watts is operated on 120 volts.

- 24 What is the resistance of the heater?
 - (1) 576,000 Ω
 - (2) 120 Ω
 - (3) 3.0 Ω
 - (4) 40. Ω
- 25 How much energy is used by this heater in 10.0 seconds?
 - (1) 1.15 J
 - (2) 40. J
 - (3) 4.8×10^3 J
 - (4) 4.8×10^4 J

Note that questions 26 through 28 have only three choices.


- 26 If the heater were replaced by one having a greater resistance, the amount of heat produced each second would
 - 1 decrease
 - 2 increase
 - 3 remain the same
- 27 If another heater is connected in parallel with the first one and both operate at 120 volts, the current in the first heater will
 - 1 decrease
 - 2 increase
 - 3 remain the same
- 28 If the original heater were operated at less than 120 volts, the amount of heat produced would
 - 1 decrease
 - 2 increase
 - 3 remain the same

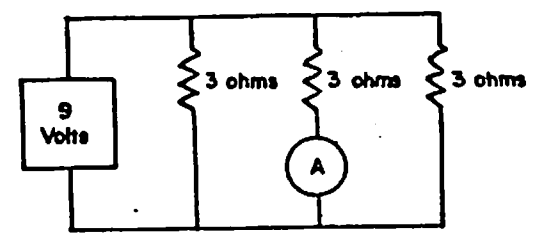29 What is the current in ammeter A in the diagram below?



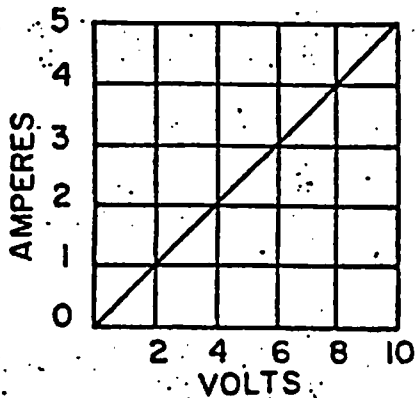- (1) 1 A
- (2) $\frac{1}{3}$ A
- (3) 3 A
- (4) 9 A

Base your answers to questions 30 through 34 on the graph below which represents data obtained by applying different potential differences to a metallic conductor at a constant temperature.



30 The resistance of the conductor is approximately

- (1) 1.0 ohm
- (2) 2.0 ohms
- (3) 0.5 ohm
- (4) 4.0 ohms

31 At 6.0 volts, what is the rate of use of energy by the conductor?

- (1) 54 watts
- (2) 18 watts
- (3) 12 watts
- (4) 6.0 watts

Note that questions 32 through 34 have only three choices.

32 If the temperature of the conductor is increased, the amount of current at 10 volts would be

- 1 less
- 2 greater
- 3 the same


33 If the length of the conductor were increased, the amount of current at 10 volts would be

- 1 less
- 2 greater
- 3 the same

34 Compared to a conductor of the same material with a larger cross-sectional area, the resistance of this conductor is

- 1 less
- 2 greater
- 3 the same

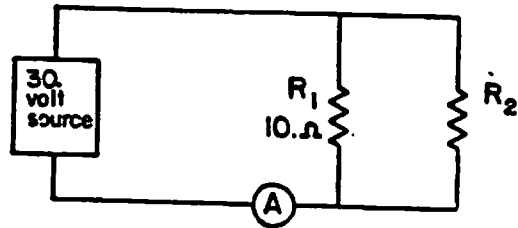Base your answers to questions 35 through 39 on the diagram below which represents two resistances (R_1 and R_2) and an ammeter connected to a constant 30.-volt source. The combined resistance of the circuit is 6.0 ohms.



35 The resistance of R_2 is equal to

- (1) 6.0 Ω
- (2) 2.0 Ω
- (3) 15 Ω
- (4) 4.0 Ω

36 Ammeter A reads

- (1) 7.5 A
- (2) 5.0 A
- (3) 3.0 A
- (4) 1.2 A

37 What power is developed in resistor R_1 alone?

- (1) 60. W
- (2) 90. W
- (3) 150 W
- (4) 250 W

Note that questions 38 and 39 have only three choices.

38 Compared to the potential difference across the source, the potential difference across R_2 is

- 1 less
- 2 greater
- 3 the same

39 If the resistance of R_2 were increased, the current through R_2 would

- 1 decrease
- 2 increase
- 3 remain the same

40 A 10-volt potential difference maintains a 2-ampere current in a resistor. The total energy expended by this resistor in 5 seconds is

- (1) 10 J
- (2) 20 J
- (3) 50 J
- (4) 100 J